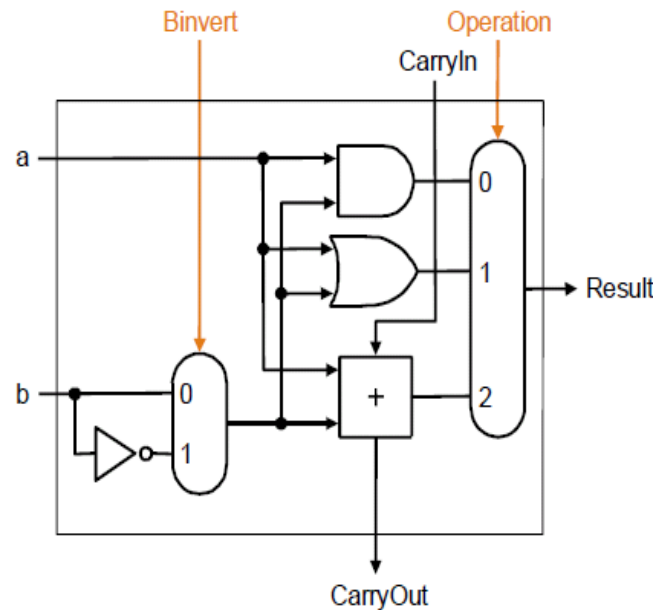


COMP2611: Computer Organization

4-bit ALU and processor in Logisim


Reminder : 1-bit ALU that does AND, OR, Addition, Subtraction₂

- ❑ The 1-bit ALU we are going to build can perform AND, OR, Addition and Subtraction operations on two 1-bit inputs.



- ❑ A 4-bit ALU can be built using 4 of the 1-bit ALUs shown above. Each 1-bit ALU will take care of the operations for exactly one bit.


- One possible design of a 4-bit ALU.

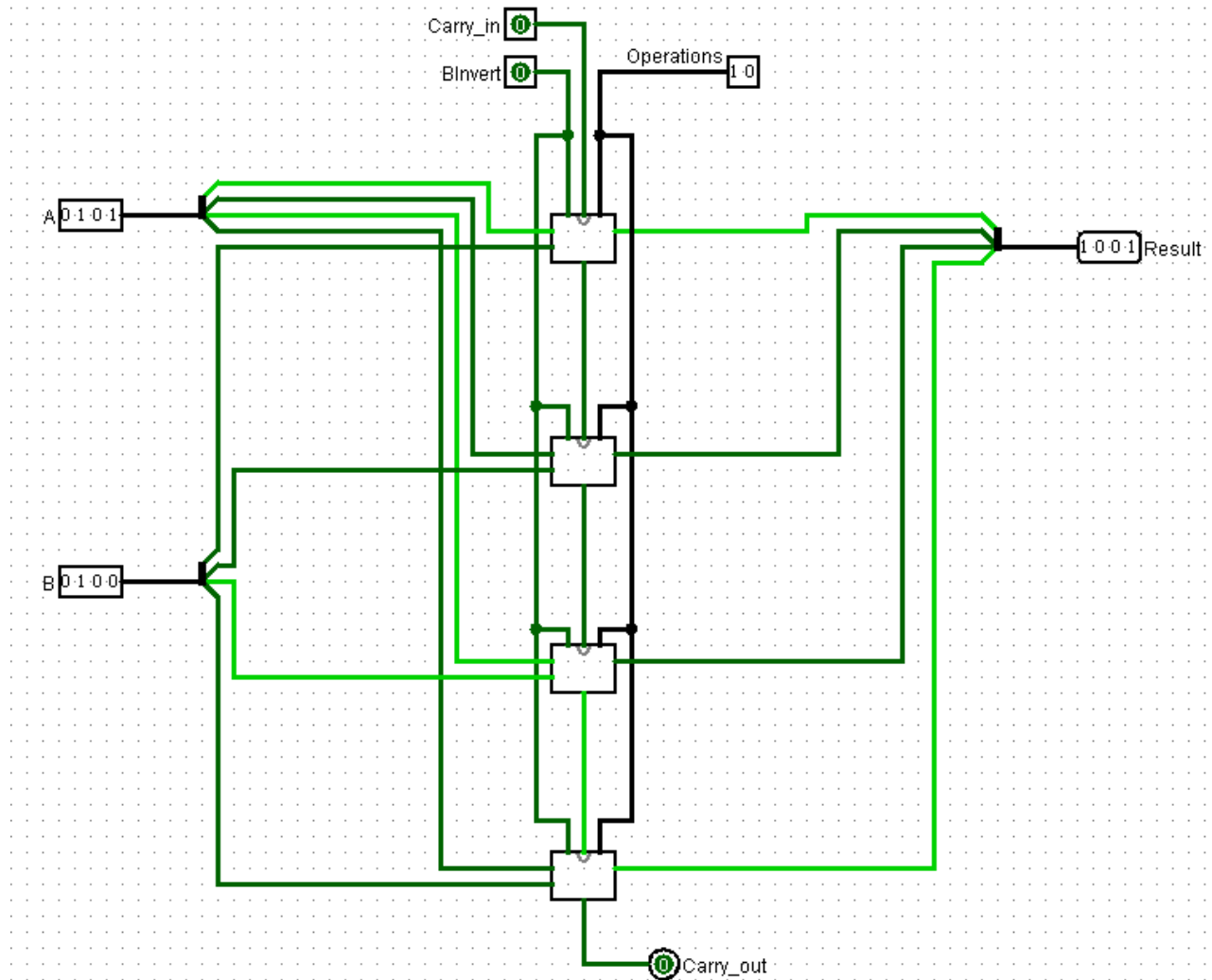

- ❑ Load the logisim files "1-bit-adder.circ", "3-input-multiplexor.circ", "1-bit-alu.circ" made in last lab, by clicking "Project->Load Library->Logisim Library";

- ❑ Drag the 1-bit-alu circuit four times into canvas for connection;
 - Pay attention to the connections of Carry_In/Carry_Out between 1-bit ALUs;
 - Pay attention to the connections of operation bits between 1-bit ALUs;
 - Pay attention to the connections of BInvert bits between 1-bit ALUs;

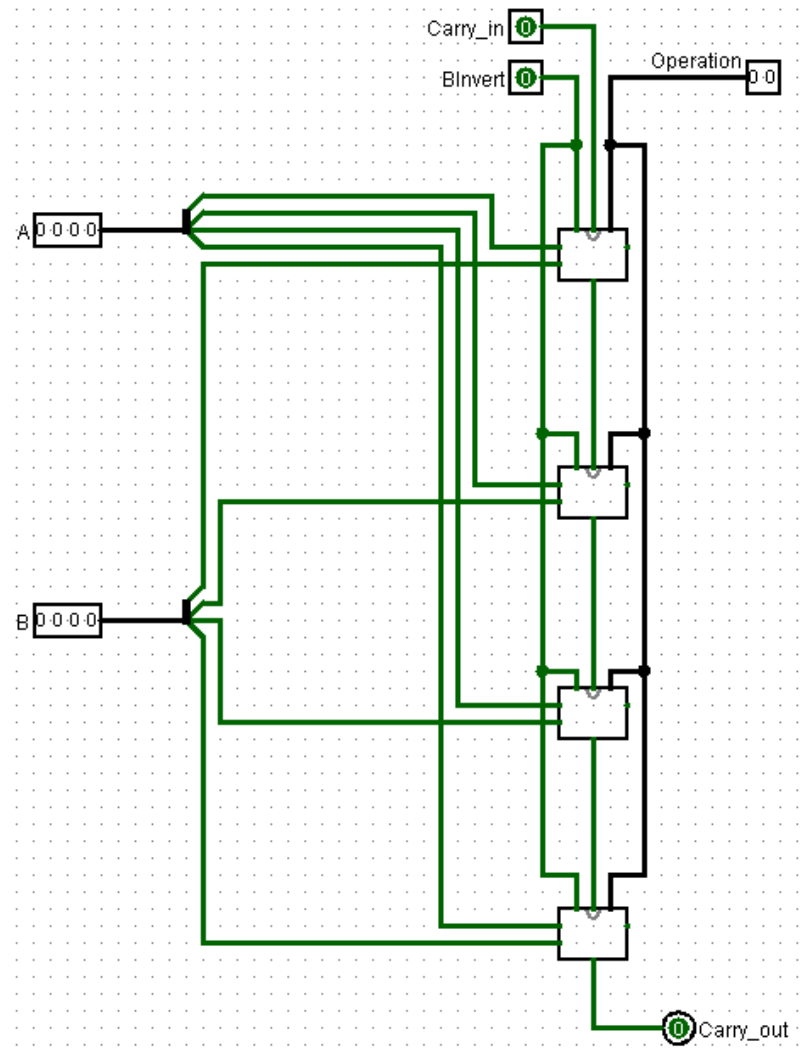- ❑ Drag two input pins "A" and "B", each as an operand with 4-bit data width;
- ❑ Connect these two input pins with four 1-bit ALUs correctly (note that splitters may be used);
- ❑ Drag an output pin as the "Carry_Out", and connect it correctly.



- ❑ Drag an output pin as "result" and connect it correctly (note that a splitter may also need to be used to facilitate the 4-bit output).
- ❑ After finishing all the connections, check the 4-bit ALU for its correctness.

- ❑ One possible design of an 8-bit processor.
- ❑ Reference link: <http://minnie.tuhs.org/CompArch/Tutes/week03.html>

